
WEBENCH® Design Report

VinMin = 20.0V
VinMax = 28.0V
Vout = 12.0V
Iout = 3.0A

Device = TPS56837HRPAR
Topology = Buck
Created = 2026-09-05 17:58:47.741
BOM Cost = $3.03
BOM Count = 16
Total Pd = 1.01W

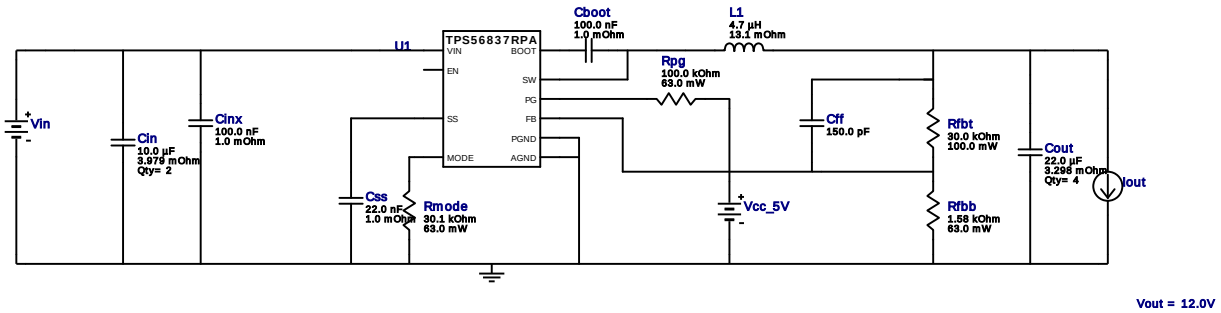Design : 1 TPS56837HRPAR
TPS56837HRPAR 20V-28V to 12.00V @ 3A





Electrical BOM


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cboot	MuRata	GRM155R71C104KA88D Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	$0.01	0402 3 mm²
Cff	Kemet	C0603C151K3GACTU Series= C0G/NP0	Cap= 150.0 pF VDC= 25.0 V IRMS= 0.0 A	1	$0.02	0603 5 mm²
Cin	Taiyo Yuden	MSASU32MSB5106KPNA01 Series= X5R	Cap= 10.0 uF ESR= 3.979 mOhm VDC= 50.0 V IRMS= 3.4821 A	2	$0.16	1210 15 mm²
Cinx	Yageo	CC0805KRX7R9BB104 Series= X7R	Cap= 100.0 nF ESR= 1.0 mOhm VDC= 50.0 V IRMS= 0.0 A	1	$0.02	0805 7 mm²
Cout	Taiyo Yuden	MSAST32MSB7226KPNB25 Series= X7R	Cap= 22.0 uF ESR= 3.298 mOhm VDC= 25.0 V IRMS= 3.7481 A	4	$0.18	1210 15 mm²
Css	MuRata	GRM155R71C223KA01D Series= X7R	Cap= 22.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A	1	$0.01	0402 3 mm²
L1	Coilcraft	XAL6060-472MEB	L= 4.7 µH 13.1 mOhm	1	$0.82	XAL6060 72 mm²
Rfbb	Vishay-Dale	CRCW04021K58FKED Series= CRCW..e3	Res= 1.58 kOhm Power= 63.0 mW Tolerance= 1.0%	1	$0.01	0402 3 mm²
Rfbt	Yageo	RC0603FR-0730KL Series= ?	Res= 30.0 kOhm Power= 100.0 mW Tolerance= 1.0%	1	$0.01	0603 5 mm²
Rmode	Vishay-Dale	CRCW040230K1FKED Series= CRCW..e3	Res= 30.1 kOhm Power= 63.0 mW Tolerance= 1.0%	1	$0.01	0402 3 mm²


Copyright © 2026, Texas Instruments Incorporated


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Rpg	Vishay-Dale	CRCW0402100KFKED Series= CRCW..e3	Res= 100.0 kOhm Power= 63.0 mW Tolerance= 1.0%	1	$0.01	0402 3 mm^2
U1	Texas Instruments	TPS56837HRPAR	Switcher	1	$1.06	RPA0010A 16 mm^2

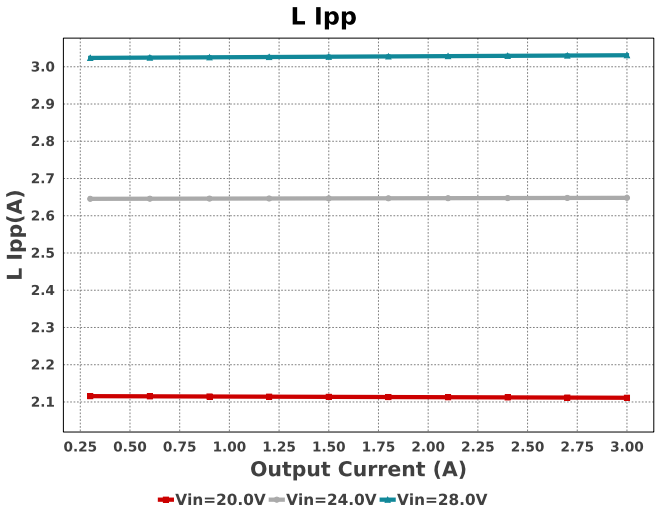


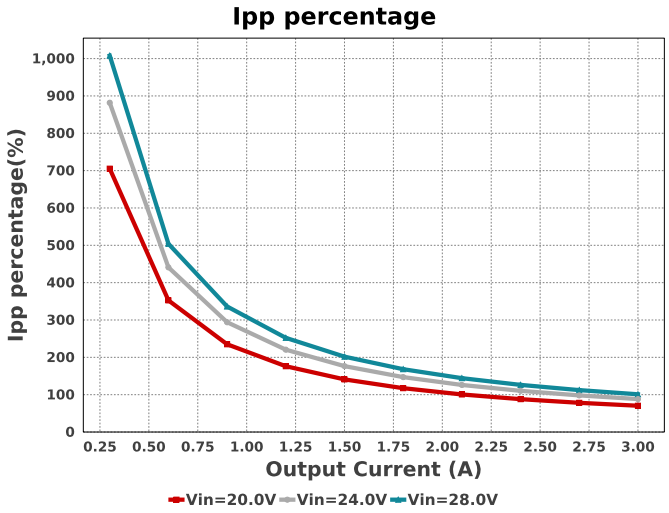

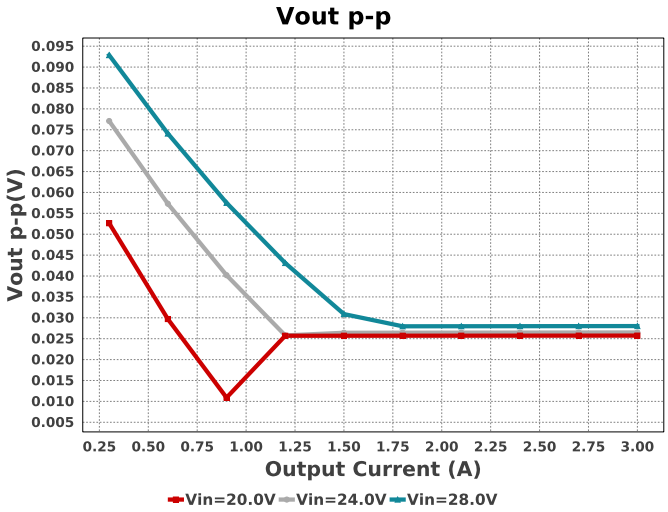


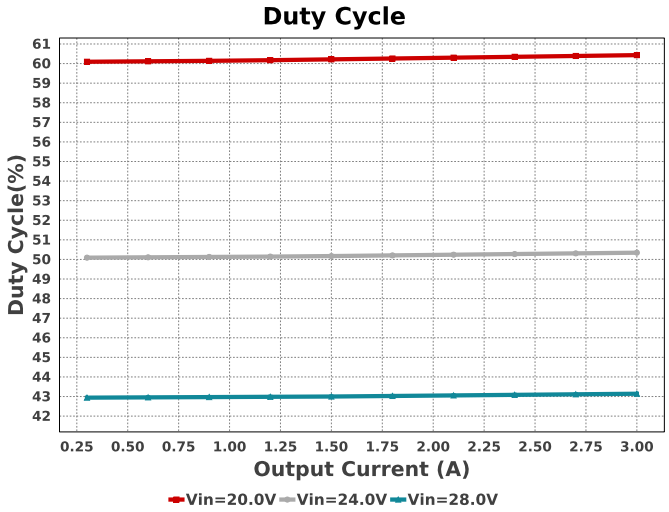


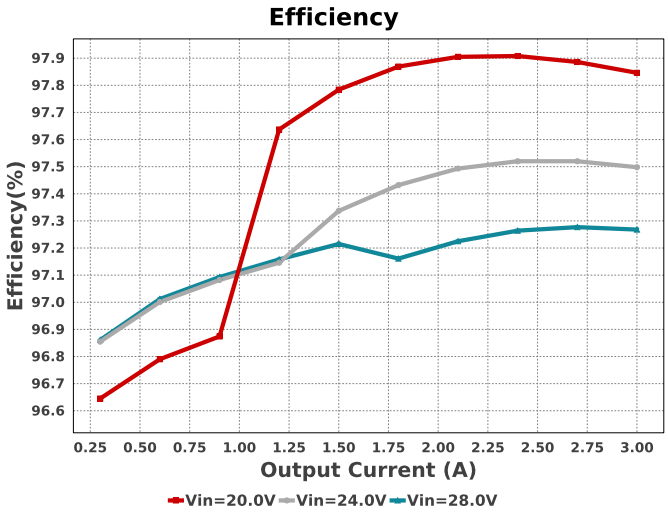


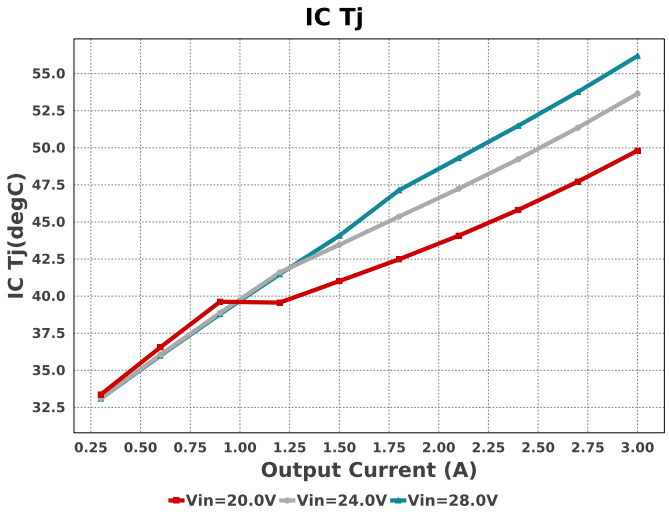


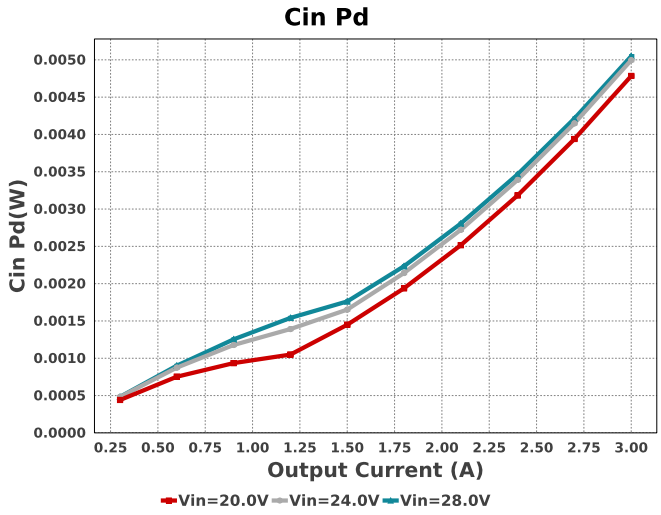
Copyright © 2026, Texas Instruments Incorporated




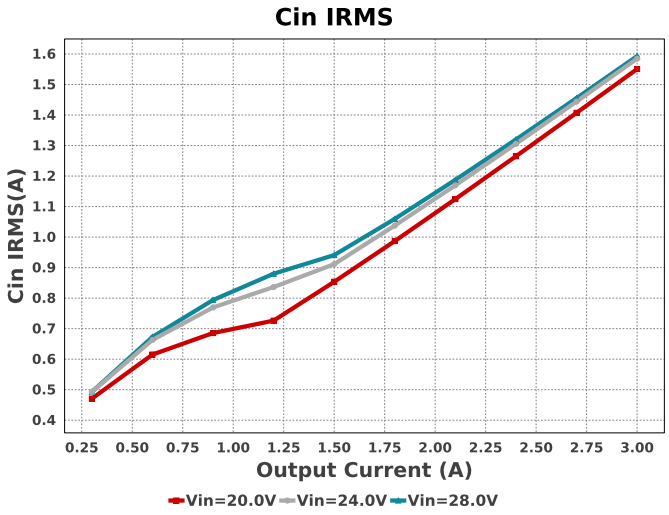

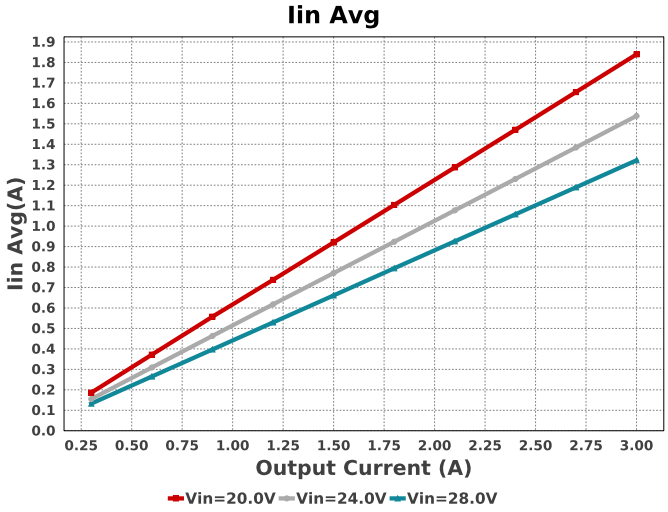


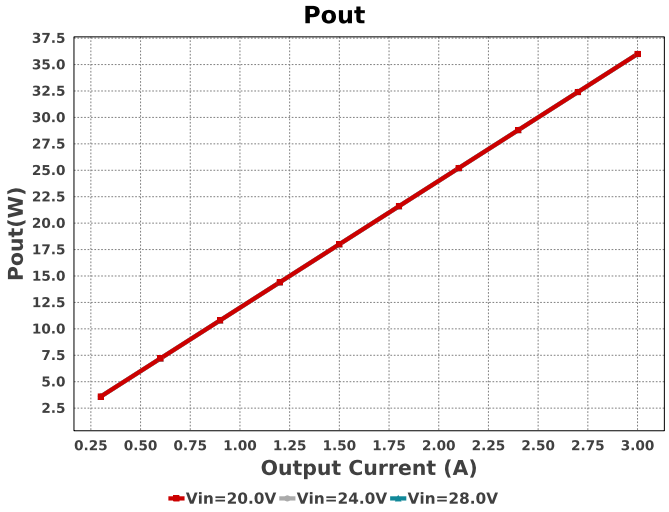


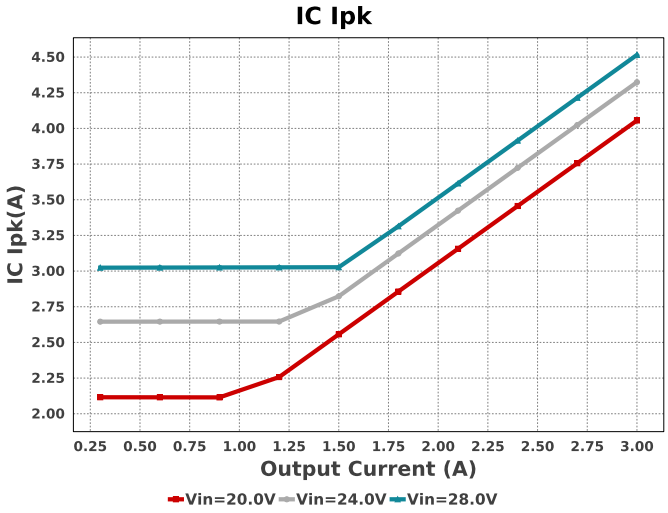


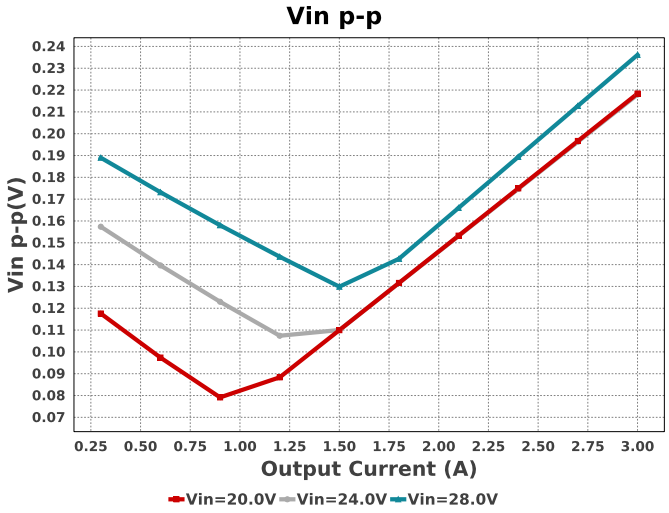


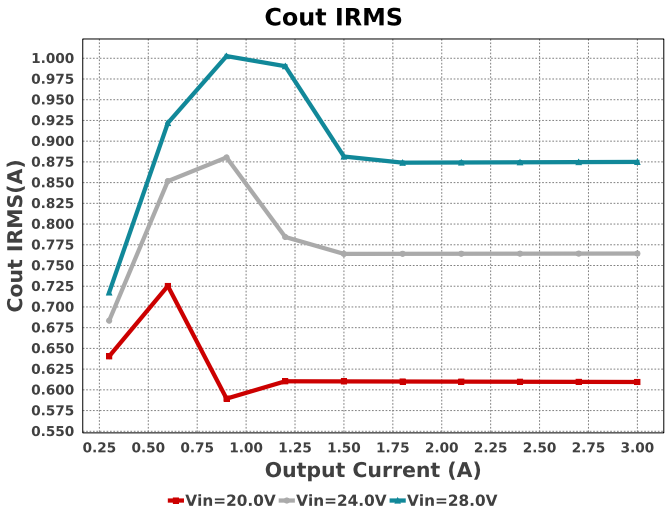
Copyright © 2026, Texas Instruments Incorporated




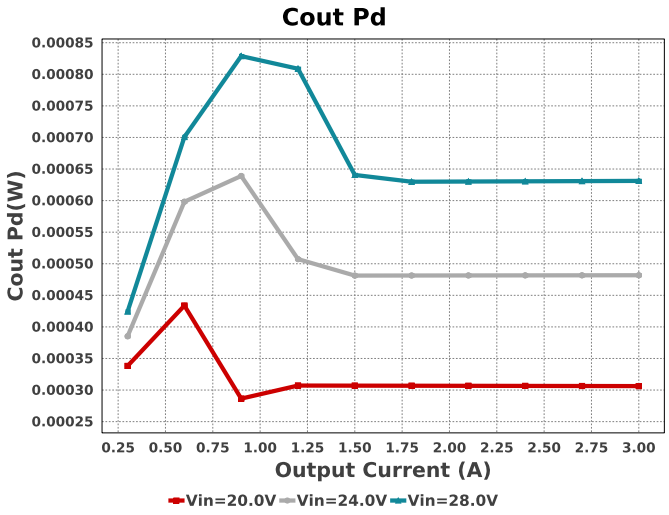

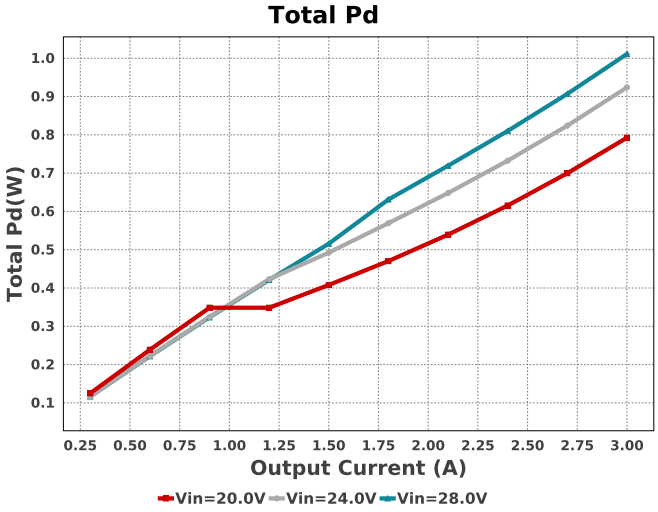

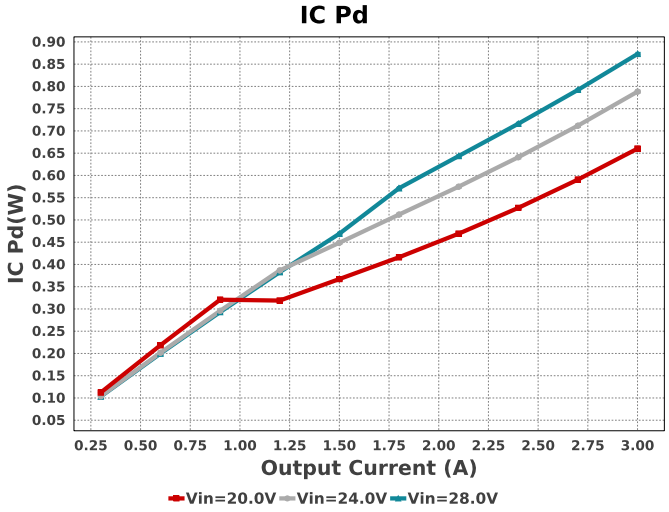

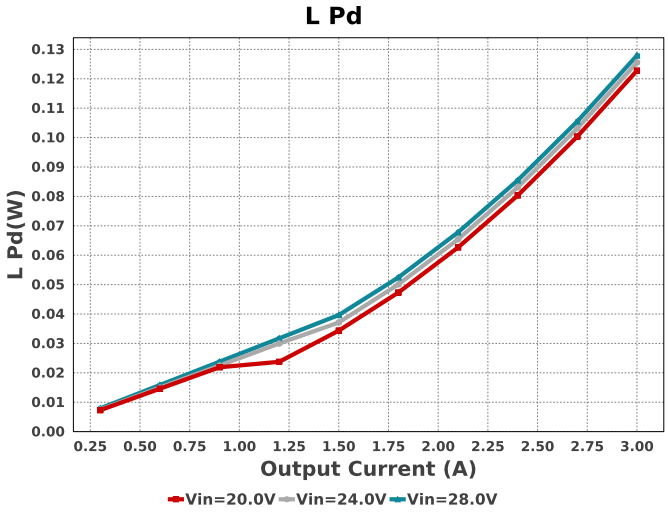

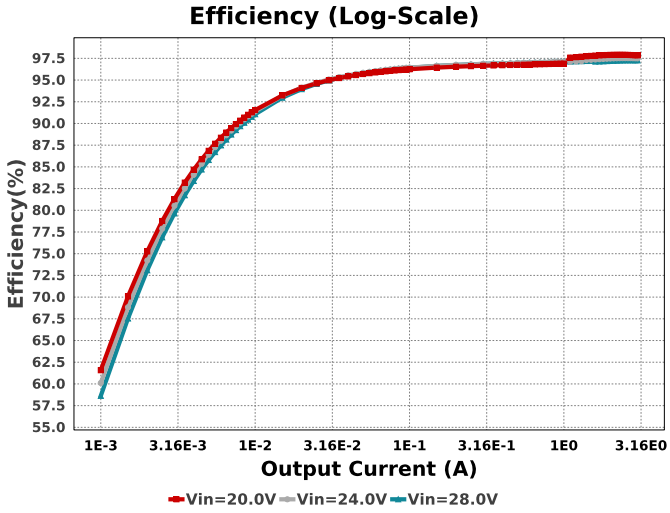

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.593 A	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	5.049 mW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	874.953 mA	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	631.19 µW	Capacitor	Output capacitor power dissipation
5.	IC Ipk	4.515 A	IC	Peak switch current in IC
6.	IC Pd	872.87 mW	IC	IC power dissipation
7.	IC Tj	56.186 degC	IC	IC junction temperature
8.	IC Tolerance	6.0 mV	IC	IC Feedback Tolerance
9.	ICThetaJA	30.0 degC/W	IC	IC junction-to-ambient thermal resistance
10.	Iin Avg	1.322 A	IC	Average input current

Copyright © 2026, Texas Instruments Incorporated

#	Name	Value	Category	Description
11.	Ipp percentage	101.031 %	Inductor	Inductor ripple current percentage (with respect to average inductor current)
12.	L Ipp	3.031 A	Inductor	Peak-to-peak inductor ripple current
13.	L Pd	127.93 mW	Inductor	Inductor power dissipation
14.	Cin Pd	5.049 mW	Power	Input capacitor power dissipation
15.	Cout Pd	631.19 µW	Power	Output capacitor power dissipation
16.	IC Pd	872.87 mW	Power	IC power dissipation
17.	L Pd	127.93 mW	Power	Inductor power dissipation
18.	Total Pd	1.011 W	Power	Total Power Dissipation
19.	BOM Count	16	System Information	Total Design BOM count
20.	Duty Cycle	43.142 %	System Information	Duty cycle
21.	Efficiency	97.268 %	System Information	Steady state efficiency
22.	FootPrint	207.0 mm^2	System Information	Total Foot Print Area of BOM components
23.	Frequency	481.518 kHz	System Information	Switching frequency
24.	Iout	3.0 A	System Information	Iout operating point
25.	Mode	CCM	System Information	Conduction Mode
26.	Pout	36.0 W	System Information	Total output power
27.	Total BOM	$3.03	System Information	Total BOM Cost
28.	Vin	28.0 V	System Information	Vin operating point
29.	Vin p-p	236.132 mV	System Information	Peak-to-peak input voltage
30.	Vout	12.0 V	System Information	Operational Output Voltage
31.	Vout Actual	11.992 V	System Information	Vout Actual calculated based on selected voltage divider resistors
32.	Vout Tolerance	2.938 %	System Information	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
33.	Vout p-p	28.022 mV	System Information	Peak-to-peak output ripple voltage

Design Inputs

Name	Value	Description
Iout	3.0	Maximum Output Current
VinMax	28.0	Maximum input voltage
VinMin	20.0	Minimum input voltage
Vout	12.0	Output Voltage
base_pn	TPS56837H	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature

Copyright © 2026, Texas Instruments Incorporated

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of Cin and Cout, and the inductance and DC resistance of L1 before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab town to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 20.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to Vin and GND. Connect a digital volt meter and a load if needed to set the minimum Iout of the design from Vout and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between Vin and GND, a load is connected between Vout and GND and a current meter is connected in series between Vout and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

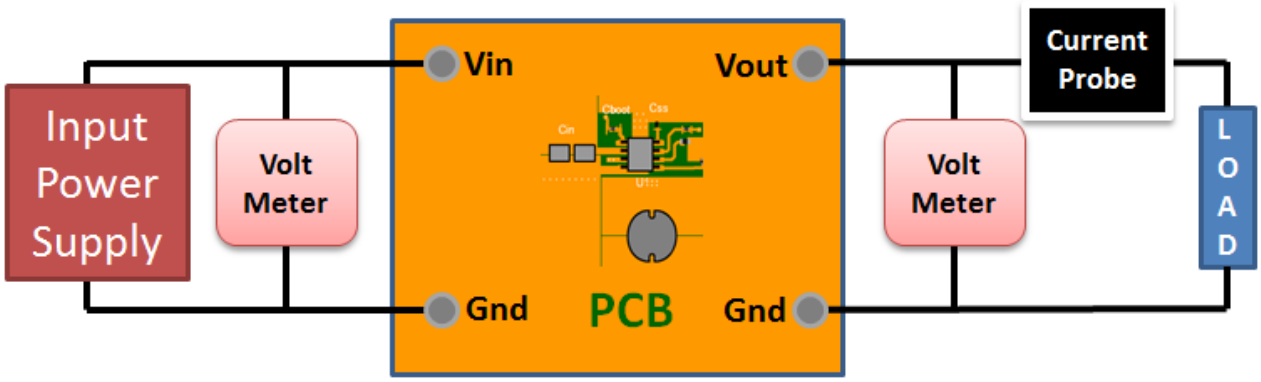

Design Assistance

1. Master key : 82336CEA7242C1512F1AAFB052B9B86E[v1]
2. **TPS56837H** Product Folder : http://www.ti.com/product/TPS56837H : contains the data sheet and other resources.

Copyright © 2026, Texas Instruments Incorporated

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.